

Avoiding Audible Noise at Light Loads When Using Leading Edge Triggered PFC Converters

John Bottrill

System Power

This application note applies to the TI average current mode, leading edge modulation PFC controllers. See Applicable Device Table for part numbers.

When using a leading edge triggered PFC the designer may find that the converter under extremely light load conditions will encounter an audible low noise.

The unit under these conditions can go into the over voltage protection (OVP) state because of the extremely light load. When this happens, the output of the current error amplifier can fall to ground because of the input offset voltage variations and the residual current from MOUT.

When the unit comes out of the OVP state, the pulse width of the converter is going to start at a maximum. Because of the integrating nature of the error amplifier, these pulses will continue for a few milliseconds. This can cause the windings of the PFC inductor to physically oscillate resulting in a periodic burst of audible noise.

A single resistor from V_{REF} to the positive input of the current error amplifier added to the circuit is sufficient to remove this problem.

The input offset voltage of the error amplifier and the multiplier zero current (I_{MOUT} , zero current) are given in the data sheet. Divide the offset voltage by the value of the resistor connecting the positive input of the current error amplifier to ground and add to this the multiplier zero current. This gives the current needed through the resistor to bias the positive input high under OVP conditions. Now divide the V_{REF} voltage by this current to get the resistor needed to connect from V_{REF} to the positive input of the current error amplifier.

The new resistor will bias the positive input high enough to keep the current error amplifier output high during OVP and because of the integrating nature of the current error amplifier, when OVP is released the unit will gradually increase the pulse width of the pulses as the current error amplifier output falls.

1 Schematic

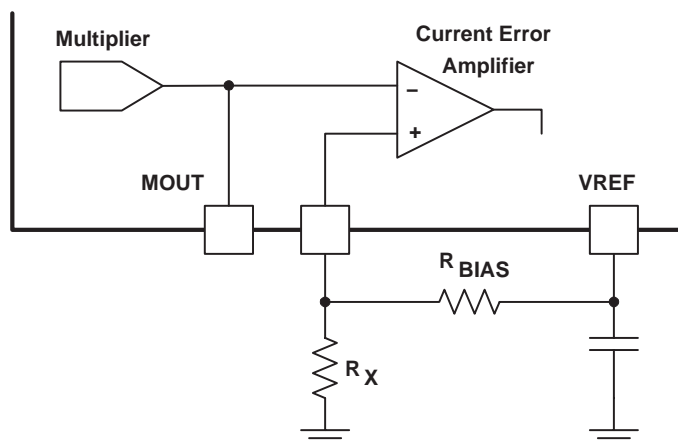


Figure 1.

Where R_X is the existing resistor from the positive input of the current error amplifier to ground,

$$I_{BIAS} = \frac{V_{OFFSET}}{R_X}$$

$$R_{BIAS} = \frac{V_{REF}}{(I_{BIAS} + I_{MOUT, \text{ zero current}})}$$

Select the nearest standard value lower than this for R_{BIAS} .

Table 1. Applicable Devices

BiCMOS Power Factor Preregulators		BiCMOS PFC/PWM Combination Controllers	
UCC2817	UCC2817A	UCC28500	UCC28510
UCC2818	UCC2818A	UCC28501	UCC28511
UCC2819	UCC2819A	UCC28502	UCC28512
UCC3817	UCC3817A	UCC28503	UCC28513
UCC3818	UCC3818A	UCC38500	UCC28514
UCC3819	UCC3819A	UCC38501	UCC28515
		UCC38502	UCC28516
		UCC38503	UCC28517

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2004, Texas Instruments Incorporated